

# Signal and Data Analysis


## Exercise 4

25.4.2008

Dr. T. Dietel, Prof. Dr. Ch. Weinheimer, Prof. Dr. J.P. Wessels
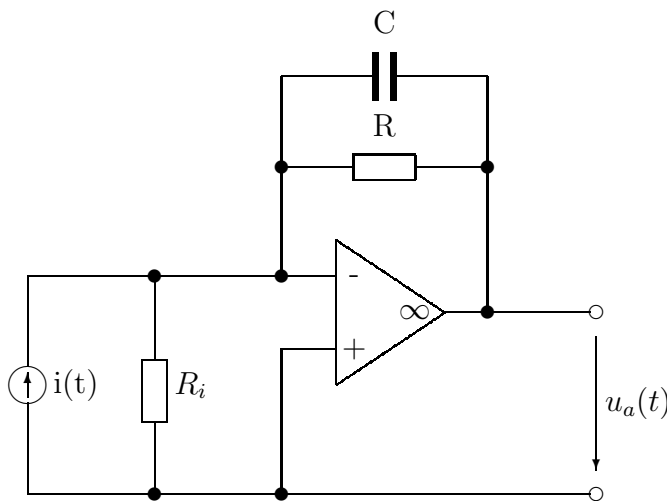
### 1 Charge-sensitive Preamplifier

Determine with the help of the Laplace transformation  $u_a(t)$  for the integrator (see below). Calculate  $u_a(t)$  using the Laplace transformation for the two different input currents  $i(t)$ :



Determine  $u_a(t)$  for

- $i(t) = Q_0\delta(t)$
- $i(t) = \frac{Q_0}{T}[\Theta(t) - \Theta(t - T)]$  assuming  $T \ll RC$ .
- Check the results using the theorems for  $t = 0$  (initial value theorem) and  $t \rightarrow \infty$  (final value theorem).


Reminder: For an ideal operational amplifier the following statements hold:

**Rule 1:** If an ideal operational amplifier is used with negative feedback in its linear regime, both inputs (inverted “-” and non-inverted “+”) are on same potential

**Rule 2:** Both inputs have infinitely high input resistance  $R_i \rightarrow \infty$
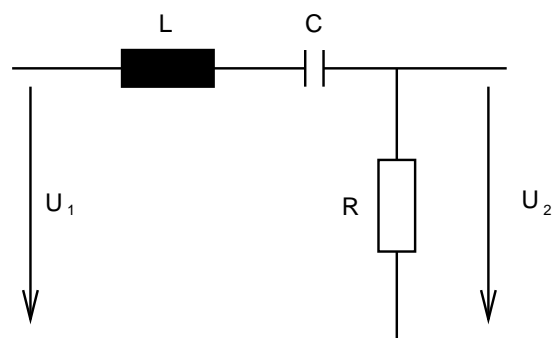
## 2 Band Filter

Determine the transfer function  $G(s)$  of the following passive filter.



Plot the Bode diagrams ( $20\text{dB } \log_{10}|G(j\omega)|$ ,  $\phi(\omega)$ ) as function of  $\log_{10}(\omega/\omega_0)$  schematically. Which kind of filter is it?